 



Design and Testbench

Tuan Nguyen-viet

Full Adder




Full Adder (2)

 

```
module full_adder (a_in, b_in, c_in, c_out, sum_out);  
  
    input [3:0] a_in, b_in;  
    input c_in;  
    output carry_out;  
    output [3:0] sum_out;  
  
    reg carry_out;  
    reg [3:0] sum_out;  
  
    always @ (a_in or b_in or c_in)  
    begin  
        {carry_out, sum_out} = a_in + b_in + c_in;  
    end  
  
endmodule
```

Full Adder (3)

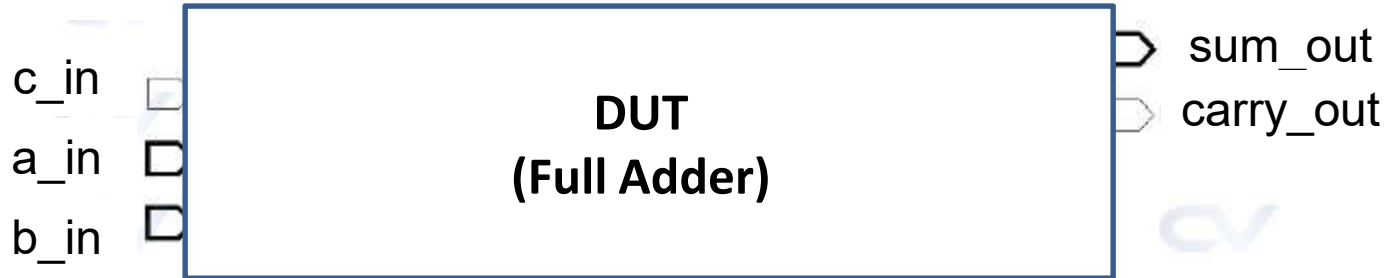

```
full_adder dut (  
    .a_in(    ),  
    .b_in(    ),  
    .c_in(    ),  
    .carry_out(    ),  
    .sum_out(    )  
);
```

Testbench

DUT




Testbench


DUT

Testbench

DUT

 

Testbench

 


```
`timescale 1 ns/10 ps
```

```
module full_adder_test; // 4-bit
```

```
reg [3:0] a, b;
```

```
reg c;
```

```
wire [3:0] sum;
```

```
wire carry;
```

```
initial
```

```
begin
```

```
    a = 4'b0000;
```

```
    b = 4'b0000;
```

```
    c = 1'b0;
```

```
    #50;
```

```
    a = 4'b0101;
```

```
    b = 4'b1010;
```

```
    // => sum=1111, carry=0
```

```
    #50;
```

```
    a = 4'b1111;
```

```
    b = 4'b0001;
```

```
    // => sum=0000, carry=1
```

```
    #50;
```

```
    a = 4'b0000;
```

```
    b = 4'b1111;
```

```
    c = 1'b1;
```

```
    // => sum=0000, carry=1
```

```
    #50;
```

```
    a = 4'b0110;
```

```
    b = 4'b0001;
```

```
    // => sum=1000, carry=0
```

```
end
```

```
endmodule
```

```
full_adder dut (  
    .a_in(    ),  
    .b_in(    ),  
    .c_in(    ),  
    .carry_out(    ),  
    .sum_out(    )  
);
```



```

`timescale 1 ns/10 ps

module full_adder_test; // 4-bit

reg [3:0] a, b;
reg c;
wire [3:0] sum;
wire carry;

full_adder dut (
    .a_in(    ),
    .b_in(    ),
    .c_in(    ),
    .carry_out(    ),
    .sum_out(    )
);

initial
begin
    a = 4'b0000;
    b = 4'b0000;
    c = 1'b0;
    #50;
    a = 4'b0101;
    b = 4'b1010;
    // => sum=1111, carry=0
    #50;
    a = 4'b1111;
    b = 4'b0001;
    // => sum=0000, carry=1
    #50;
    a = 4'b0000;
    b = 4'b1111;
    c = 1'b1;
    // => sum=0000, carry=1
    #50;
    a = 4'b0110;
    b = 4'b0001;
    // => sum=1000, carry=0
end
endmodule

```

```
`timescale 1 ns/10 ps
```

```
module full_adder_test; // 4-bit
```

```
reg [3:0] a, b;
```

```
reg c;
```

```
wire [3:0] sum;
```

```
wire carry;
```

```
full_adder dut (  
    .a_in(a),  
    .b_in(b),  
    .c_in(c),  
    .carry_out(carry),  
    .sum_out(sum)  
);
```

```
initial
```

```
begin
```

```
    a = 4'b0000;
```

```
    b = 4'b0000;
```

```
    c = 1'b0;
```

```
    #50;
```

```
    a = 4'b0101;
```

```
    b = 4'b1010;
```

```
    // => sum=1111, carry=0
```

```
    #50;
```

```
    a = 4'b1111;
```

```
    b = 4'b0001;
```

```
    // => sum=0000, carry=1
```

```
    #50;
```

```
    a = 4'b0000;
```

```
    b = 4'b1111;
```

```
    c = 1'b1;
```

```
    // => sum=0000, carry=1
```

```
    #50;
```

```
    a = 4'b0110;
```

```
    b = 4'b0001;
```

```
    // => sum=1000, carry=0
```

```
end
```

```
endmodule
```

Thank You